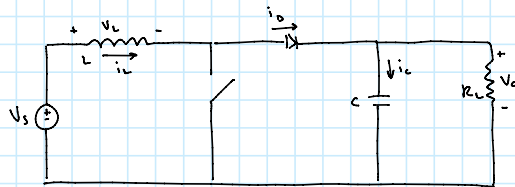


Boost Converter Analysis

Wednesday, September 9, 2020 11:00 AM




Switch closed:

- diode reverse biased
- $V_L = V_s = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt} = \frac{V_s}{L}$
constant

$$\Delta i_L = \frac{\Delta i_L}{\Delta t} = \frac{V_s}{L} \Delta t \rightarrow \Delta i_L = \frac{V_s \Delta t}{L}$$

current increases linearly

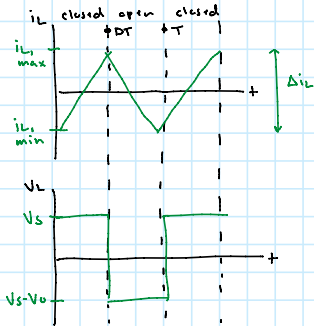

Switch open:

- DC inductor current cannot change instantaneously, diode becomes forward biased to provide a path for the inductor current
- $V_L = V_s - V_o = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt} = \frac{V_s - V_o}{L}$
constant

$$\Delta i_L = \frac{\Delta i_L}{\Delta t} = \frac{V_s - V_o}{L} \Delta t \rightarrow \Delta i_L = \frac{(V_s - V_o)(1-D)T}{L}$$

current decreases linearly

Steady-state operation,

net change in i_L must be zero:

$$\Delta i_{L, \text{closed}} + \Delta i_{L, \text{open}} = 0$$

$$\frac{V_s \Delta t}{L} + \frac{(V_s - V_o)(1-D)T}{L} = 0$$

$$V_s(D + (1-D)) - V_o(1-D) = 0$$

$$V_o = \frac{V_s}{1-D}$$

average inductor voltage must be zero:

$$V_L = V_s D + (V_s - V_o)(1-D) = 0$$

$$V_o = \frac{V_s}{1-D}$$


verify ✓

this would allow for V_o to approach ∞ , however non-ideal components have losses which prevent this

Output Voltage Ripple

- finite capacitance yields fluctuation in output voltage (ripple)
- Peak-to-peak output voltage ripple can be calculated from

Capacitor current waveform

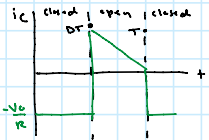

change in capacitor charge:

$$\Delta Q_C = \frac{V_o}{R} \Delta t = C \Delta V_o$$

$$\Delta V_o = \frac{V_o \Delta t}{RC} \rightarrow \frac{V_o}{RC} = \frac{D}{RC}$$

Capacitance in terms of output voltage:

$$C = \frac{D}{R \left(\frac{V_o}{V_s} \right) f}$$

Voltage ripple due to equivalent series resistance (ESR):

$$\Delta V_{o, \text{ESR}} = \Delta i_C \cdot r_C = I_{L, \text{max}} \cdot r_C$$

Power

- average power supplied by source =
- average power absorbed by R_L

$$P_o = \frac{V_o^2}{R} = \frac{V_o^2}{V_s^2} \cdot \frac{V_s^2}{R} = \left(\frac{V_o}{V_s} \right)^2 \cdot \frac{V_s^2}{R}$$

$$P_i = V_s I_s = V_s I_L$$

- I_L can be expressed as

$$I_L = \frac{V_s}{(1-D)^2 R} = \frac{V_o^2}{V_s^2} \cdot \frac{V_s}{R} = \frac{V_o^2}{V_s R}$$

$$I_{L, \text{min}} = I_L - \frac{\Delta i_L}{2} = \frac{V_s}{2(1-D)^2 R} - \frac{V_s \Delta t}{2L}$$

$$I_{L, \text{max}} = I_L + \frac{\Delta i_L}{2} = \frac{V_s}{2(1-D)^2 R} + \frac{V_s \Delta t}{2L}$$

- Continuous inductor current denotes > 0 ,

$$I_{L, \text{min}} = 0 = \frac{V_s}{2(1-D)^2 R} - \frac{V_s \Delta t}{2L} \rightarrow \frac{V_s}{2(1-D)^2 R} = \frac{V_s \Delta t}{2L} \rightarrow \frac{V_s \Delta t}{2L} = \frac{V_s \Delta t}{2L}$$

- minimum inductance value/operating frequency for continuous operation:

$$L_{\text{min}} = \frac{D(1-D)^2 R}{2} \rightarrow L_{\text{min}} = \frac{D(1-D)^2 R}{2f} \rightarrow \frac{V_s \Delta t}{\Delta i_L} = \frac{V_s \Delta t}{\Delta i_L}$$

Example

$V_o = 30V, V_s = 12V, \text{ripple} \leq 1\%, R = 50\Omega, f = 25kHz$

- $D = 1 - \frac{V_s}{V_o} = 0.6$
- $L_{\text{min}} = \frac{D(1-D)^2 R}{2(25kHz)} = 96\mu H, L = 120\mu H$
- $I_L = \frac{V_s}{(1-D)^2 R} = 1.5A$
 $I_{L, \text{min}} = 0.3A$
 $I_{L, \text{max}} = 2.7A$
- $\Delta i_L = \frac{V_s \Delta t}{L} = 1.2A$
- $C \geq \frac{D}{R \left(\frac{V_o}{V_s} \right) f} = \frac{0.6}{50(0.01)25 \times 10^3} = 48\mu F$

Example

$V_o = 8V, I_o = 1A, V_s = 2.7-4.2V, \text{ripple} \leq 2\%, \Delta i_L \leq 40\% I_{L, \text{avg}}$

- $D = 1 - \frac{V_s}{V_o} = 0.663, 0.475$
- $I_L = \frac{V_o I_o}{V_s} = 2.96A, 1.9A$
- $\Delta i_L = 0.4(I_L) = 1.19A, 0.762A$
- $L = \frac{V_s D}{\Delta i_L} = 7.5\mu H, 13.1\mu H$

$$C = \frac{D}{R \left(\frac{V_o}{V_s} \right) f} = \frac{D}{R \left(\frac{V_o}{V_s} \right) f} = ?$$

- $\Delta i_L = \frac{V_s D}{L f} = 0.683A$
- $I_{L, \text{max}}, 1.7V = I_L + \frac{\Delta i_L}{2} = 3.3A$
- $I_{L, \text{max}}, 4.2V = I_L + \frac{\Delta i_L}{2} = 2.78A$
- $\Delta V_{o, \text{ESR}} = \Delta i_C \cdot r_C = I_{L, \text{max}} r_C = 3.3$
 $r_C = 0.16V = 48m\Omega$

Inductor Resistance (non-ideal inductor)


$$P_s = P_o + P_{\text{loss}}$$

$$V_s I_L = V_o I_o + I_L^2 r_L \rightarrow \text{series resistance of inductor}$$

$$I_o = I_L(1-D) \text{ diode current } = I_L \approx \text{zero}$$

$$V_o = \left(\frac{V_s}{1-D} \right) \left(\frac{1}{1 + r_L / (R(1-D)^2)} \right)$$

Efficiency

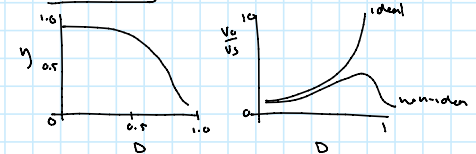

$$\eta = \frac{P_o}{P_o + P_{\text{loss}}} = \frac{V_o^2 / R}{V_o^2 / R + I_L^2 r_L} = \frac{1}{1 + r_L / (R(1-D)^2)}$$